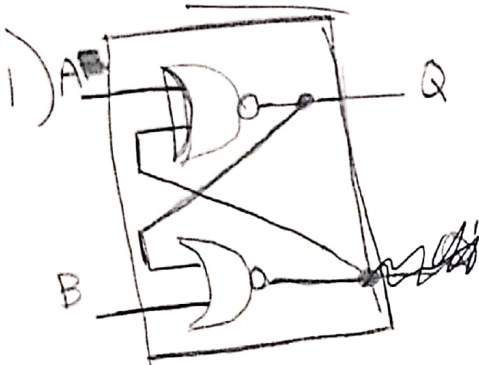


Quiz - Latches

- 1) (2 pts) Using nor gates, please design a simple latch. Use inputs A, B, and output Q.
- 2) (3 pts) For the latch, indicate what states lead to set ($Q=1$), reset ($Q=0$), and store.
- 3) (1 pt) Also identify the state that leads to uncontrolled oscillation.
- 4) (4 pts) Using logic gates, create an "interface" for the raw latch that does the following:
 - a. User inputs J & K, interface outputs to A & B on the raw latch
 - b. When $J=1, K=0$, the latch is set
 - c. When $J=0, K=1$, the latch is unset (to zero)
 - d. When $J=0, K=0$, the latch holds (does not change value)
 - e. When $J=1, K=1$, the latch toggles (Q becomes not- Q)

SEE BACK FOR ANSWERS



2) Truth table for the simple latch:

A	B	Q
0	0	Toggle
0	1	1 (set)
1	0	0 (reset)
1	1	Toggle

I think 00 is a toggle

3) The NOR's switch back and forth between true and false as one of their inputs keeps flipping.

4) Truth table for the J-K interface:

A	B	Q
0	0	Toggle?
0	1	1 (set)
1	0	0 (reset)
1	1	Toggle

Built under the assumption that the following truth table holds

A	B	Q
0	0	Toggle
0	1	1 (set)
1	0	0 (reset)
1	1	Toggle

a) $J=A, K=B$

b) $J=\bar{A}, K=B$

c)

e) $J=\bar{A}, K=\bar{B}$

A	K	Q
0	0	1
0	1	0
1	0	1
1	1	0


B	K	Q
0	0	1
0	1	0
1	0	1
1	1	0

b) $10 \rightarrow 10$

c) $01 \rightarrow 11$

d)

e) $11 \rightarrow 00$

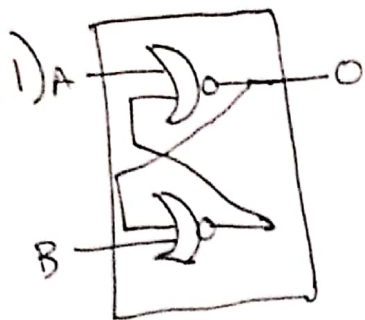


2)

A	B	Q
0	0	oscillates
0	1	1 (set)
1	0	0 (reset)
1	1	store nope

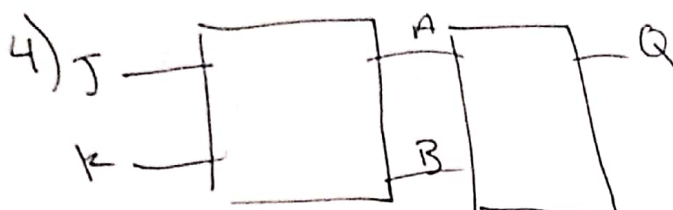3)

00 causes w/ existing Q to flip back and forth a lot really fast, or, it stores.



Built assuming the truth table above is true

b) latch set on 10

c) latch reset on 01

d) hold on 00

e) toggle on 11

+ 3


A	K	Q
0	0	1
0	1	1
1	0	?

B	K	Q
0	0	1
0	1	0
1	1	?

I'm not sure how to toggle this without oscillation. But I do think this would avoid a 00.

$$A = \bar{J}$$


$$B = K$$

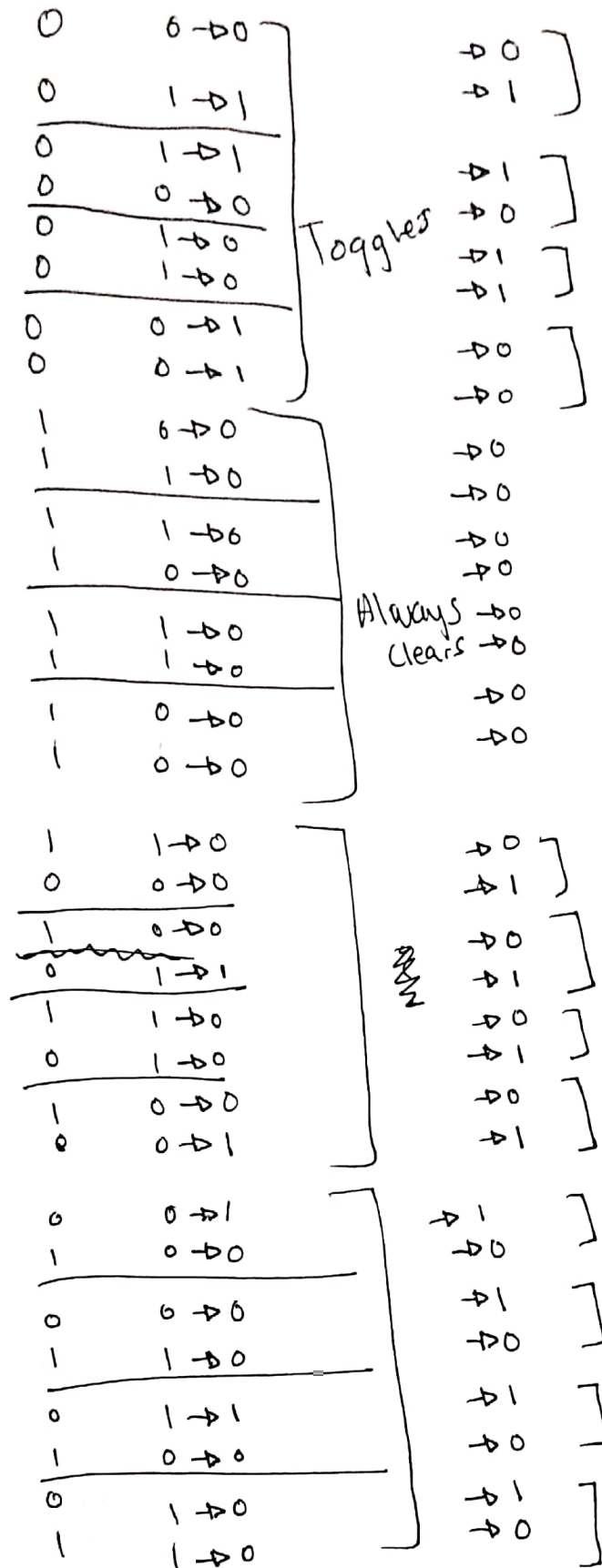

10 pts



Quiz - Latches

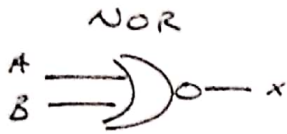- 1) (2 pts) Using nor gates, please design a simple latch. Use inputs A, B, and output Q.
- 2) (3 pts) For the latch, indicate what states lead to set ($Q=1$), reset ($Q=0$), and store.
- 3) (1 pt) Also identify the state that leads to uncontrolled oscillation.
- 4) (4 pts) Using logic gates, create an "interface" for the raw latch that does the following:
 - a. User inputs J & K, interface outputs to A & B on the raw latch
 - b. When $J=1, K=0$, the latch is set
 - c. When $J=0, K=1$, the latch is unset (to zero)
 - d. When $J=0, K=0$, the latch holds (does not change value)
 - e. When $J=1, K=1$, the latch toggles (Q becomes not- Q)




A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

A	B	Q	
0	0	Q_0	old value of Q
0	1	1	set
1	0	0	Reset
1	1	0	avoid, leads to oscillation if you go from 00 \rightarrow 11 state

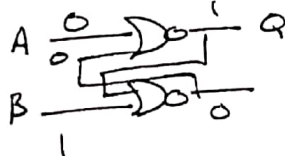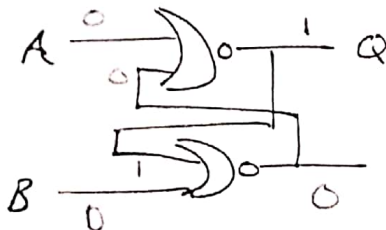

oscillation

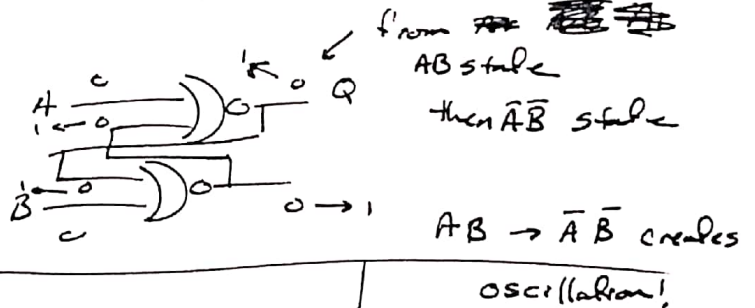

4) Interface:

User inputs	Wants	so, map to latch command
0 0	hold	A B 0 0
1 0	set	0 1
0 1	unset (clear)	1 0
1 1	toggle	$Q_0 \bar{Q}_0$ ← old Q

if $Q_0 = 1$
want $Q_1 = 0$ so clear command!

~~so, could you say~~
 ~~$A = JK + Q_0$~~
~~And could you say~~
 ~~$B = JK + \bar{Q}_0$~~

so

$$A = JK + Q_0$$

$$B = JK + \bar{Q}_0$$