

Electronics

Ch 2 2, 10, 15, 18, 22, 25, 35, 37

32

7/4/4/4/1/1


7/4/4

Adam Stammer




$$Q.2) V_1(t) = 1 \cos(20\pi t) + 20 \sin(120\pi t) \quad V_2(t) = -0.1 \cos(20\pi t) + 20 \sin(120\pi t)$$
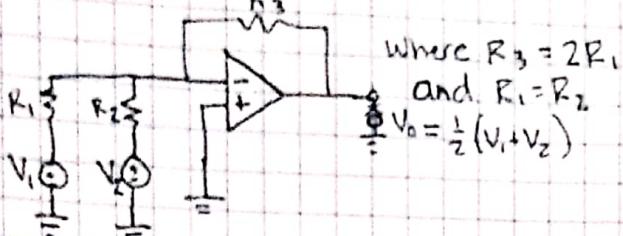
$$\text{Common mode: } \frac{1}{2}(V_1 + V_2) = \frac{1}{2}(40 \sin 120\pi t) = \boxed{20 \sin 120\pi t} \quad \boxed{20 \sin 120\pi t}$$


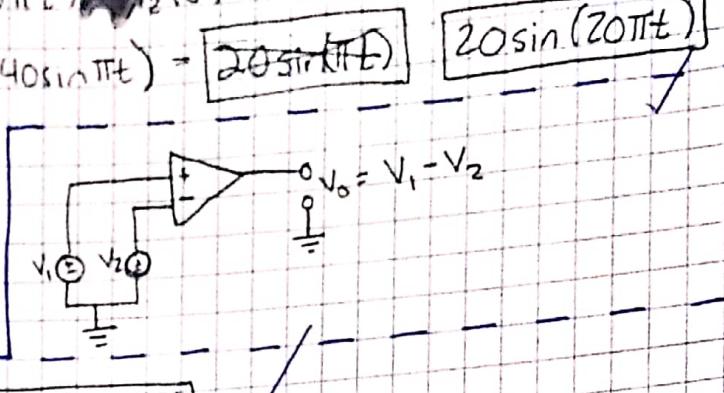
$$\text{where } R_3 = 2R_1 \text{ and } R_1 = R_2 \\ V_0 = \frac{1}{2}(V_1 + V_2)$$



$$\text{differential signal: } (V_1 - V_2) = .2 \cos(120\pi t)$$

$$Q.10) \text{ Find } V_o \quad 2mA \xrightarrow{1k\Omega} \text{sum} \xrightarrow{3k\Omega} \text{out} \quad \frac{V_o - V_-}{R_F} = I_F \quad \frac{V_o - 0}{1000\Omega} = 2mA \quad V_o = 1000(2mA) = \boxed{2 \text{ Volts}}$$

and the signal goes into the neg pin since the feed back is negative, it should be negating

$$\text{Find } V_o \quad 2mA \xrightarrow{1k\Omega} \text{sum} \xrightarrow{3k\Omega} \text{out} \quad \frac{V_o - V_-}{R_F} = I_F \quad \frac{V_o - 5V}{3000\Omega} = 2mA \quad V_o = 3000(2mA) + 5V = \boxed{6 + 5 = 11 \text{ Volts}}$$

$$\text{Find } V_o \quad 4V \xrightarrow{1k\Omega} \text{sum} \xrightarrow{3k\Omega} \text{out} \quad \frac{V_o - 0}{1k\Omega} = I_F \quad \frac{V_o - 0}{1k\Omega} = \frac{V_o}{1k\Omega}$$

$$V_o - 1V - 3k\Omega I_F = 1k\Omega I_F = V_o \quad I_F = \frac{V_o - 0}{1k\Omega} = \frac{V_o}{1k\Omega}$$

$$V_o - 1V - 3V_o - V_o = 0 \quad 4 - 1 - 3k(0) = V_o = \boxed{13 \text{ Volts}}$$

~~but current shouldn't flow through the top or bottom branch so I don't like my answer~~

$$\text{Find } V_o \quad \frac{V_o - 0}{15k\Omega} = 3mA \quad V_o = 3mA(15k\Omega) = \boxed{45 \text{ Volts}}$$

~~Again, current shouldn't be flowing through the 15kΩ resistor so I don't like this answer either.~~

$$+5 - 2 = \boxed{3 \text{ Volts}}$$

Again our only flowing current is that of the load resistor so I'm not sure where to start even.

$$5 \xrightarrow{I} \text{sum} \xrightarrow{1k\Omega} \text{out} \quad V_o = ? \text{ No clue}$$

5.) R_1 and R_2 have tolerances of $\pm 1\%$. What is the gain tolerance of this inverting amplifier?

We've already solved an inverting amplifier to be $A = \frac{R_2}{R_1}$
so let's look at the extremes.

an increased R_1 with a decreased R_2


$$\frac{R_2(0.99)}{R_1(1.01)} \approx A(0.98)$$

a decreased R_1 with an increased R_2

$$\frac{R_2(1.01)}{R_1(0.99)} \approx A(1.02) \quad \checkmark$$

So we see a gain tolerance range of roughly $\pm 2\%$. I would guess that the resistance tolerances add together.

18.)

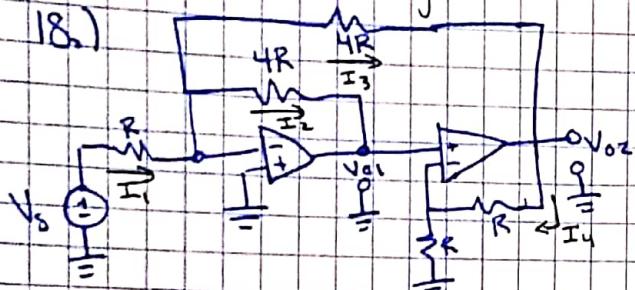

Since no current goes in V_- or V_+ , we can say that $I_1 = I_2 + I_3$

Sub in variables and values to see that

$$\frac{V_1 - V_s}{R} = \frac{V_{o1} - V_1}{4R} + \frac{V_{o2} - V_1}{4R} \Rightarrow 4V_s = V_{o1} + V_{o2}$$

Now we can also make a statement regarding I_4 . Since no current is going through the op amps V_{-2} we can say that I_4 is constant through both of those final resistors. So,


$$\frac{V_{o2} - V_{o1}}{R} = \frac{V_{o1} - 0}{R} \Rightarrow V_{o2} - V_{o1} = V_{o1} \Rightarrow V_{o2} = 2V_{o1}$$

2 equations and 2 unknowns. Simple substitution.

$$-4V_s = V_{o1} + 2V_{o1} = 3V_{o1} \Rightarrow V_{o1} = (-4/3)V_s$$

$$V_{o2} = 2(-4/3)V_s = V_{o2} = (-8/3)V_s \quad \checkmark$$

22.) Find V_o

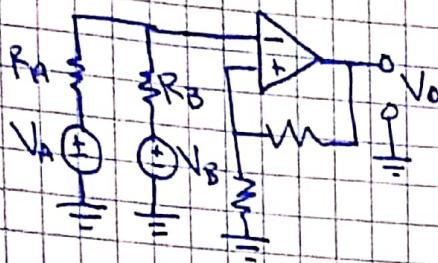

First lets look at the voltage coming into V_-
we can redraw it as follows
 V_A with no current flowing to V_-
so lets nodally analyze it

Now lets look at the output
using what we found at the input.

$$\frac{V_o - V_-}{R_2} = \frac{V_- - 0}{R_1}$$

$$V_o = \frac{(V_-)R_2}{R_1} + V_- = V_- \left(\frac{R_2}{R_1} + 1 \right)$$

$$= V_- \left(\frac{R_2 + R_1}{R_1} \right)$$

$$V_o = \left(\frac{R_2 + R_1}{R_1} \right) \left(V_A \left(\frac{R_B}{R_A + R_B} \right) + V_B \left(\frac{R_A}{R_A + R_B} \right) \right)$$

$$\frac{V_- - V_A}{R_A} = \frac{V_B - V_-}{R_B}$$

$$R_A V_B - R_A V_- = R_B V_- - R_B V_A$$


$$R_A V_B + R_B V_A = R_B V_- + R_A V_-$$

$$V_- = V_B \left(\frac{R_A}{R_A + R_B} \right) + V_A \left(\frac{R_B}{R_A + R_B} \right)$$

so the input on V_- is an adding voltage divider. neat.

which to me looks like a weighted summer with amplification that is non-inverting. With the right resistors we could find averages with this circuit I do believe.

25.)

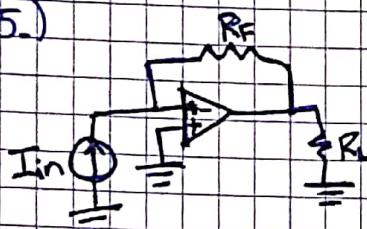

a) Find V_o

↳ all current from I_{in} must be going through R_F

$$V_o = -I_{in} * R_F$$

b) Output Impedance: $R_F \parallel 0$

c) Input Impedance: 0

d) ~~non-inverting amplifier~~ Transresistance since it puts out a V_o based on a I_{in} . It also has $(R_F \text{ and } R)$


35.) Design a single op amp with a gain of -100 and no resistor smaller than $1k\Omega$. Try to minimize resistance

The most basic of inverting amplifiers follow $V_o = -V_s \left(\frac{R_F}{R_1} \right)$
so if $R_F = 100,000\Omega$ and $R_1 = 1,000\Omega$, we would achieve our goal of -100 gain and have big enough resistors. $100,000\Omega$ is a pretty large resistance though.

$$A_{v, \text{min}} = \frac{V_o}{V_{in}} = - \left(\frac{R_2}{R_1} + \frac{R_3}{R_1} + \frac{R_4 R_2}{R_1 R_3} \right)$$

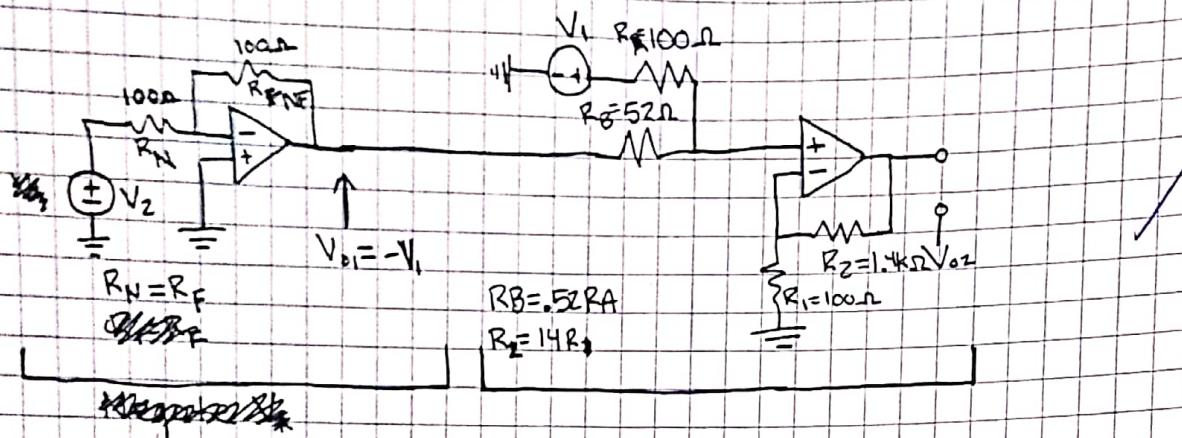35.) Design circuit such that $V_o = A_1 V_1 + A_2 V_2$
and $A_1 = 5$ and $A_2 = -10$.

So lets use a summing op amp circuit combined with an inverter.



Negate V_2

Weighted Summer $15(V_A(.33) + V_B(.66))$

Accepting that V_2 has been negated already, lets focus on the weighted summer

We already solved this summing circuit to be $V_o = \left(\frac{R_z + R_f}{R_f}\right) \left(V_A \left(\frac{R_f}{R_A + R_B}\right) + V_B \left(\frac{R_A}{R_A + R_B}\right)\right)$

We'll simplify the notation such that

$$X = \left(\frac{R_z + R_f}{R_f}\right), Y = \left(\frac{R_B}{R_A + R_B}\right), \text{ and } Z = \left(\frac{R_A}{R_A + R_B}\right)$$

To achieve gains of 5 on A and 10 on B (since it's already negated), we just need XY to equal 5 and XZ to equal 10.

Looking at the equations, Y and Z will never be greater than 1 so let's work the other way and find those proportions based on X.

$5+10=15$ so I'll keep it simple and say that $X=15$. With this we can say that $Y = \frac{5}{15} = .33$ and $Z = \frac{10}{15} = .66$.

Now all we need to do is select one resistor in the R_1, R_2 set and another in the R_A, R_B set and solve based on our X, Y, Z equations.

See back of page for work.

| | |
|-------------------|--------------------|
| $R_A = 100\Omega$ | $R_B = 52\Omega$ |
| $R_1 = 100\Omega$ | $R_2 = 1.4k\Omega$ |
| $R_N = 100\Omega$ | $R_F = 100\Omega$ |

For convenience I'll choose R_1 and R_A to both be 100Ω

We know that

$$X = \frac{R_Z + R_1}{R_1} = \frac{R_Z + 100}{100} \text{ and we need it to equal } 15$$

so $\frac{R_Z + 100}{100} = 15 \quad R_Z = 1500 - 100 = 1.4k\Omega$

Thus ~~R_A~~ $R_1 = 100\Omega$ and $R_Z = 1.4k\Omega$

We also know that

$$Z = \frac{R_A}{R_A + R_B} = \frac{100}{100 + R_B} \text{ and we need it to equal } .66$$

so $\frac{100}{100 + R_B} = .66 \quad R_B = \frac{100}{.66} - 100 \approx 52\Omega$

Thus $R_A = 100\Omega$ and $R_B \approx 52\Omega$




Electronics
Homework 4
Ch 2: 39, 47, 51, 75, 77

4/4/4 " (20)

Adam Stammer

39.

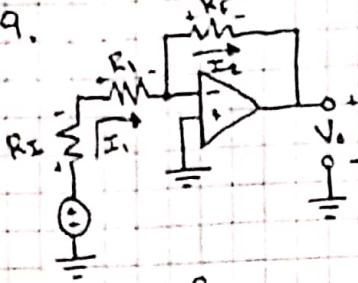

$R_I = [1000\Omega, 1M\Omega]$ Design this circuit (R_1 and R_F) such that $A_v = -20 \pm 15\%$. Assume resistor tolerances of $\pm 5\%$.

Start by solving for V_o .

$$I_1 = I_2 \Rightarrow \frac{V_s - V_o}{R_2 + R_1} = \frac{V_o - V_g}{R_F}$$

$$V_o = -V_s \left(\frac{R_F}{R_1 + R_F} \right)$$

so, $\left(\frac{R_F}{R_1 + R_F} \right) = 20 \pm 15\%$. Add in

$$\left(\frac{R_F}{R_1 + 1000} \right) = 20(1.15) \quad \text{and} \quad \left(\frac{R_F}{R_1 + 1M} \right) = 20(-.85)$$



now add in our resistor tolerances,

$$\left(\frac{R_F(1.05)}{R_1(.99) + 1000} \right) = 20(1.15) \quad , \quad \left(\frac{R_F(.99)}{R_1(1.05) + 1000} \right) = 20(-.85)$$

With two equations and two unknowns we can solve via substitution.

$$R_F = 17(R_1(.99) + 1000) / 1.05 \\ = \frac{17(.99)R_1 + 17,000}{1.05}$$

$$R_1 = \frac{(R_F(.99) - 1M)}{1.05}$$

$$= R_F \left(\frac{.99}{23(1.05)} \right) - \frac{1M}{1.05}$$

$$R_F \approx 44502113.31106$$

$$R_F \approx 44.502113 M\Omega$$

$$R_1 = \frac{(17(.99)R_1 + 17000)}{1.05} \left(\frac{.99}{23(1.05)} \right) - \frac{1M}{1.05}$$

$$R_1 = (16.029R_1 + 16190.48)(0.040994) - \frac{1M}{1.05}$$

$$R_1 = .65709R_1 + 663.71 - \frac{1M}{1.05}$$

$$R_1 = \frac{663.71 - 1M}{.34291}$$

$$R_1 \approx 2775414.08061 \approx 2.775414 M\Omega$$

Checking this answer we expect $\left(\frac{R_F}{R_1 + 499500} \right)$ to equal our exact 20 gain goal. I actually found these resistor values to achieve a $\pm 15.2\%$ tolerance around a gain of ≈ 13.9 which is significantly lower than our design requirements.

New Answer:

$$R_1 = 948595 M\Omega \quad R_2 = 199.3005 M\Omega$$

47.) DC Gain of 100

Cascading amps with gain of 10

$$A_{OL} = A_v = 100$$

$$GBP = A_{OL} \cdot f_{BOL} = 10^4$$

$$f_{BOL} = \frac{10^4}{100} = 10^4 \text{ Hz}$$

$$A_{OL}(f) = \frac{A_{OL}}{1 + j\left(\frac{f}{f_{BOL}}\right)} = \frac{A_{OL}}{1 + j\left(\frac{f}{10^4}\right)}$$

$$f_{BOL} = \frac{10^6}{10} = 10^5 \text{ Hz} \quad A_{OL}(f) = \frac{A_{OL}}{1 + j\left(\frac{f}{10^5}\right)}$$

$$A_{OL}(f) = \left(\frac{A_{OL}}{1 + j\left(\frac{f}{10^4}\right)} \right) \left(\frac{A_{OL}}{1 + j\left(\frac{f}{10^5}\right)} \right)$$

$$= \left(\frac{10}{1 + j\left(\frac{f}{10^4}\right)} \right) \left(\frac{10}{1 + j\left(\frac{f}{10^5}\right)} \right) = \frac{100}{(1 + j\left(\frac{f}{10^4}\right))^2} = \frac{100}{1 + 2j\left(\frac{f}{10^4}\right) - \left(\frac{f}{10^5}\right)^2}$$

$$= \frac{100}{\frac{f^2 + 10^{10}}{10^{10}} + 2j\left(\frac{f}{10^5}\right)}$$

Complex conjugate to take further?

Step.



51.) Skewrate at 100kHz sin wave, amplitude of 5 Volts

$$SR = 2\pi f V_{OMAX} = 2\pi(100000)(5) = 3.14 * 10^6 \text{ V/S}$$


$$= 3.14 \text{ V/μS}$$

2μF

75.) $V_s(t) (V_{0.1s})$

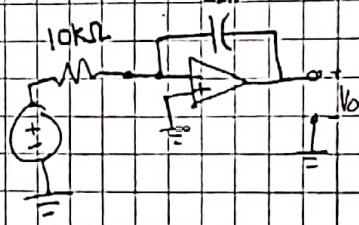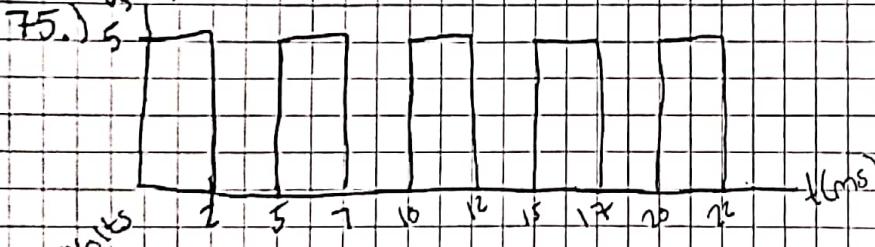

Sketch V_o over time
(ms=0, ms=2s)

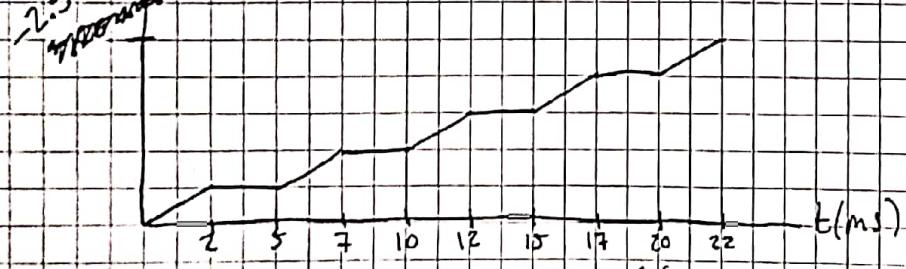

What if $V_o = -10$?

↳ How many pulses have gone through?

$$10 / 5 = 20 \text{ pulses}$$

~~10 / 5 = 2000 pulses~~ ← too many

Robotic Arm Displacement


10cm \rightarrow 1 Volt

Design circuit such that $1\text{m/s} \rightarrow 1\text{Volt}$, $2 \rightarrow 1\text{Volt}$
and another circuit such that $1\text{m/s}^2 \rightarrow 1\text{Volt}$

$$\frac{1\text{ Volt}}{1\text{ meter}} = \frac{x\text{ Volts}}{1\text{ meter}} : x = \frac{1}{1} * 1 = 10$$

So 1 meter of displacement corresponds to 10 Volts.

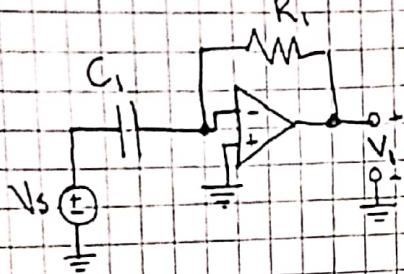Velocity is the derivative of displacement so let's use a differentiator



$$V_1 = R_1 \frac{d(V_s)}{dt}$$

$$V_1 = R_1 C_1 \frac{d(10x)}{dt}$$

$$1\text{m/s} = R_1 C_1 \frac{d(10x)}{dt}$$

$$V_s = \text{displacement} \cdot \frac{\text{Volts}}{\text{meter}}$$


$$V_s = x \left(\frac{10}{1} \right) = 10x$$

$$R_1 C_1 = \frac{1}{10}$$

$$R_1 = \frac{1}{0.1 \times 10^{-6}} = 1M\Omega$$

So let's choose $C_1 = 0.1\text{nF}$
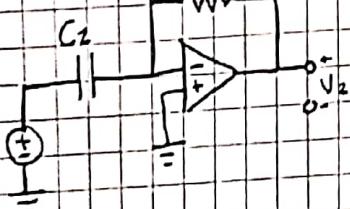
$$R_1 (0.1 \times 10^{-6}) = \frac{1}{10}$$



Now if we differentiate again we will have acceleration

Keep $g = 9.81$

1.6. 44.1 kHz @ 16 bits

4/4/4/4/4/4
24


Adam Stammer
Electronics HW #1

$$44.1 \text{ K} * 16 = 705,600 \text{ bits/s} \cong 86.13 \text{ MB/s}$$

$$2^{16} = 65,536 \text{ amplitude zones}$$

$$\frac{5 - (-5)}{2^{16}} = 152.6 \mu\text{V}$$

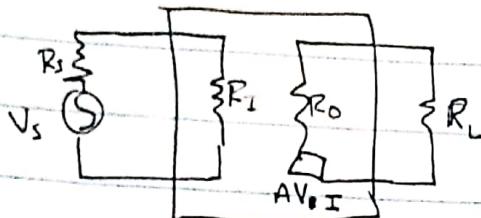1.15 $V_s = 2 \text{ mV}$ $R_s = 50 \text{ k}\Omega$ $A_{voc} = 100$ $R_I = 100 \text{ k}\Omega$ $R_o = 4 \text{ }\Omega = R_L$



$$V_{oI} = \left(\frac{R_I}{R_I + R_s} \right) V_s \quad V_o = \left(\frac{R_L}{R_L + R_o} \right) AV_{oI}$$

$$V_o = \left(\frac{R_L}{R_L + R_o} \right) A_{voc} \left(\frac{R_I}{R_I + R_s} \right) V_s = \left(\frac{4}{4+4} \right) (100) \left(\frac{100 \text{ k}}{100 \text{ k} + 50 \text{ k}} \right) (.002)$$

$$= \left(\frac{1}{2} \right) (100) \left(\frac{2}{3} \right) (.002) = \frac{100}{3} (.002) = \frac{200}{3} \text{ mV}$$

$$A_{vs} = \frac{V_o}{V_s} = \frac{(200/3) \text{ mV}}{2 \text{ mV}} = 33.\overline{33} /$$

$$A_v = \frac{V_o}{V_I} = \frac{(200/3) \text{ mV}}{(200/100) \text{ mV}} = 50 /$$

$$I_I = \frac{V_s}{R_s + R_I} = \frac{2 \text{ mV}}{50 \text{ k} + 100 \text{ k}} \approx \frac{4}{3} * 10^{-8}$$

$$I_L = \frac{V_o}{R_L} = \frac{200/3}{4} = \frac{50}{3} \text{ mA} = \frac{50}{3} * 10^{-3}$$

$$A_I = I_L / I_I = \frac{50/3}{4/3} * \frac{10^{-3}}{10^{-8}} = 12.5 * 10^5 /$$

$$A_p = A_v * A_I = 50 (12.5 * 10^5) = 625 * 10^5 = 6.25 * 10^7$$

1.16


$$A_{voc} = 1, V_s = 5 \text{ Volts}, R_s = 100k\Omega, R_i = 1M\Omega, R_o = 100\Omega, R_L = 50\Omega$$

$$V_I = V_s \left(\frac{R_i}{R_i + R_s} \right) = 5 \left(\frac{1M}{1M + 100k} \right) = 5 (.90909) \approx 4.5455 \text{ Volts}$$

$$V_A = G_{oc} V_I = 1 (4.5455) = 4.5455 \text{ Volts}$$

$$V_o = V_A \left(\frac{R_L}{R_L + R_o} \right) = 4.5455 \left(\frac{50}{100+50} \right) \approx 1.5152 \text{ Volts}$$
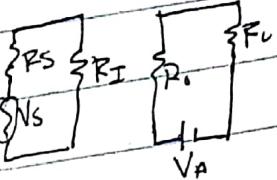
$$P_o = \frac{V_o^2}{R_L} = \frac{1.5152^2 \text{ Volts}}{50 \Omega} \approx .045917 \text{ Watts}$$



$$V_{L2} = V_s \left(\frac{R_L}{R_L + R_s} \right) = 4.5455 \left(\frac{50}{100+50} \right) \approx 1.5152 \text{ Volts}$$

$$P_{o2} = \frac{V_{L2}^2}{R_L} = \frac{1.5152^2 \text{ Volts}}{50 \Omega} \approx .045917 \text{ Watts}$$



So even with a voltage gain of unity, the power increases substantially. It seems especially helpful when the signal

this is valid b/c 2 resistors in series. Not parallel

1.17 $R_i = 75\Omega, V_s = 5 \mu\text{V}, V_o = 5\text{V}, R_L = 8\Omega$

$$P = \frac{V^2}{R} \text{ so, } P = \frac{5^2}{8\Omega} \text{ Volts}$$

$$P_i = \frac{(5 \mu\text{V})^2}{75\Omega} \text{ and } P_i = \frac{5^2}{75\Omega} \text{ Volts}$$


$$= 6.667 * 10^{-8} \text{ Watts}$$

$$A_p = \frac{P_o}{P_i} = \frac{3.125}{6.667 * 10^{-8}} \approx 46875000$$

$$P_o = \frac{25}{8} = 3.125 \text{ Watts}$$

ce.

| | A_{voc} | R_i | R_o |
|--------|-----------|------------|-------------|
| 1.21 A | 100 | $3k\Omega$ | 400Ω |
| B | 500 | $1M\Omega$ | 20Ω |

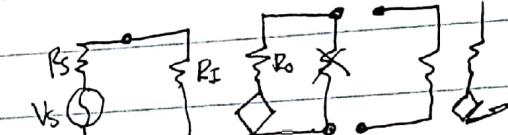

$$V_{i1} = \frac{R_{i1}}{R_{i1} + R_{s1}} V_s \quad V_{o1} = A_1 V_{i1} \left(\frac{R_{i2}}{R_{o1} + R_{i2}} \right) = V_{i2}$$

$$V_{o2} = A_2 V_{i2} = A_2 A_1 \left(\frac{R_{i1}}{R_{i1} + R_{s1}} \right) V_s \left(\frac{R_{i2}}{R_{o1} + R_{i2}} \right)$$

$$= 50000 \left(\frac{3k}{3k + R_{s1}} \right) \left(\frac{20}{400 + 20} \right) \approx 49980.008 \left(\frac{3k}{3k + R_{s1}} \right)$$

A \rightarrow B

B \rightarrow A

$$= 50000 \left(\frac{1m}{1m + R_{s1}} \right) V_s \left(\frac{3k}{3k + 20} \right)$$

$$\approx 49608.87417 \left(\frac{1m}{1m + R_{s1}} \right) V_s$$

At specific
load condition

| | A _{Voc} | Input Resistance | Output Resistance |
|--------|------------------|------------------|-------------------|
| 24D. A | 1 | 10MΩ | 4kΩ |
| B | 5 | 1kΩ | 1Ω |
| C | 10 | 20hΩ | 100Ω |

$$V_s = 20mV$$

$$R_s = 2M\Omega$$

$$R_L = 20\Omega$$

1 Watt 20Ω Load $P = \frac{V^2}{R}$

$$I = \frac{V}{R}$$

$$V = \sqrt{20} = 2\sqrt{5}$$

≈ 4.47 Volts output

$$A_{v_o} \frac{4.47}{20mV} = 223.5$$

1. We want an input resistance much higher than our source resistance and only A is higher at 10MΩ. So let's start with A.
2. We want our last amplifier to do the opposite and have an internal resistance smaller than the load resistance. B is the closest we can get to that so lets end with B.
3. For the intermediary amplifier we want something with a high voltage gain so lets use C. But, how many? If we temporarily forget power loss of internal resistance and look simply at our open circuit gain of 10, then $V_{ocn} = 0.2 * 10^n$, n being the number of class C amplifiers. Our goal is 4.47 Volts or higher and when $n=3$, $V_{ocn} = 20$. We also disregarded the first and last amplifier so I'm going to estimate a need for 3 intermediate C amplifiers. Thus A-C-C-C-B

Small Signal Analysis

Adam Stammer

Ch 4 # 42, 45, 51, 56

42) $B=100$ $I_{CQ}=1mA, .1mA, 1\mu A$ npn in active region

Find g_m and r_T

$$g_m = \frac{I_{EQ}}{V_T}$$

$$I_{EQ} = I_{BQ} + I_{CQ}$$

$$I_{CQ} = \beta I_{BQ} \rightarrow I_{BQ} = \frac{I_{CQ}}{\beta}$$

$$I_{EQ} = \frac{I_{CQ}}{\beta} + I_{CQ}$$

$$g_m = \frac{\frac{I_{CQ} + \beta I_{CQ}}{\beta}}{V_T} = \frac{I_{CQ}(1+\beta)}{\beta V_T}$$

$$g_m = .03885 @ I_{CQ} = 1mA$$

$$= .003885 @ I_{CQ} = .1mA$$

$$= .00003885 @ I_{CQ} = 1\mu A$$


$$r_T = (\beta+1) \frac{V_T}{I_{EQ}} = (\beta+1)/g_m$$

$$r_T = 67.6 \Omega @ I_{CQ} = 1mA$$

$$= 676 \Omega @ I_{CQ} = .1mA$$

$$= 67600 \Omega @ I_{CQ} = 1\mu A$$


45)

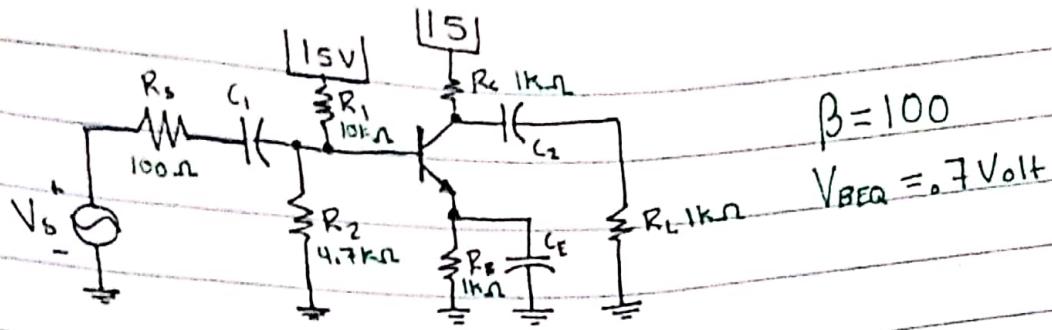

$$R_s = 100 \Omega, R_1 = 10k\Omega, R_2 = 4.7k\Omega, R_c = 1k\Omega, R_E = 1k\Omega, R_L = 1k\Omega$$

Find I_{CQ} , then r_π Find $A_v, A_{vo}, Z_{in}, A_i, G$, and Z_o

DC Capacitors open circuit

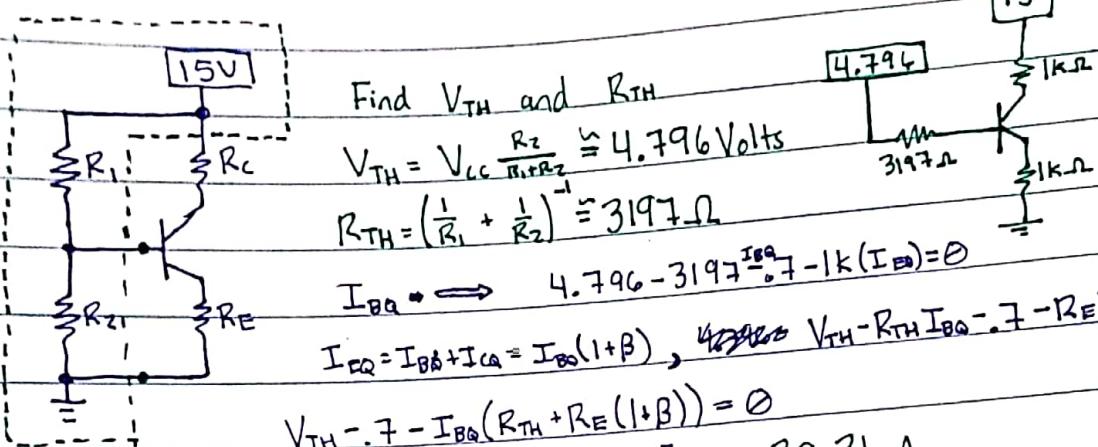

$$I_{BQ} = I_{BB} + I_{CQ} = I_{BB}(1+\beta) \rightarrow V_{TH} - R_{TH} I_{BQ} - 7 - R_E I_{BQ}(1+\beta) = 0$$

$$V_{TH} - 7 - I_{BQ}(R_{TH} + R_E(1+\beta)) = 0$$

$$I_{BQ} = \frac{V_{TH} - 7}{R_{TH} + R_E(1+\beta)} = \frac{4.796 - 7}{3197 + 1000(1+100)} = 39.31 \mu A$$

$$V_{TH} = 3197 I_{BQ}$$

~~$V_{TH} - R_{TH} I_{BQ} - 7 - R_E I_{CQ} = 0 \quad 15 - 1k I_C - V_{CE} - 1k I_E = 0$~~


$$I_{CQ} = \frac{I_{BQ}}{\beta} = \frac{39.31 \mu A}{100} = 3.93 mA$$

$$I_{EQ} = I_{CQ} + I_{BQ} \approx 3.97 mA$$

$$15 - 1000 I_{CQ} - V_{CE} - 1000 I_{EQ} = 0$$

$$r_\pi = (\beta + 1) \frac{V_T}{I_{EQ}} \quad V_{CE} = 15 - 1000(I_{CQ} + I_{EQ}) = 7.1 Volts$$


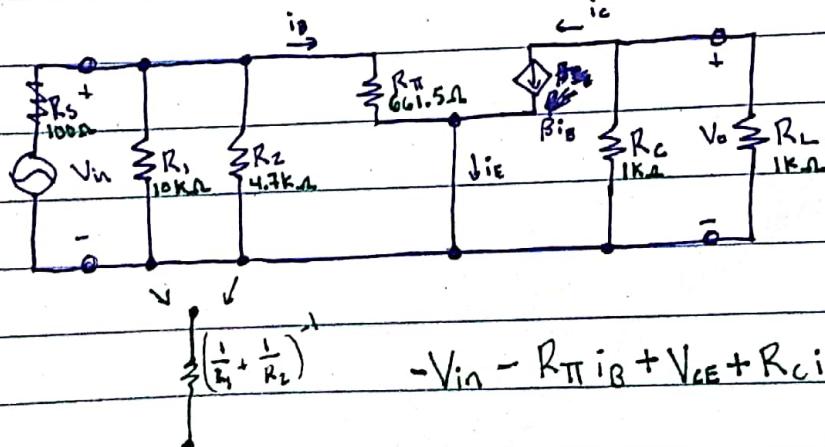
$$= (101) \left(\frac{0.026}{3.93mA} \right) \approx 661.46 \Omega \quad \text{so yeah probably active mode}$$



$$A_{v1} = \frac{V_o}{V_i} = \frac{\beta R_L'}{R_{in}} = \frac{\beta R_L'}{R_{in}} = \frac{100 \left(\frac{1}{10k\Omega} + \frac{1}{10k\Omega} \right)^{-1}}{601.5} = \frac{50000}{601.5} = 75.5858$$

$$A_{v2} = \frac{V_o}{V_i} = \frac{\beta R_L}{R_{in}} = \frac{100 \left(10k\Omega \right)}{601.5} = \frac{1000}{601.5} = 151.1716$$

51.

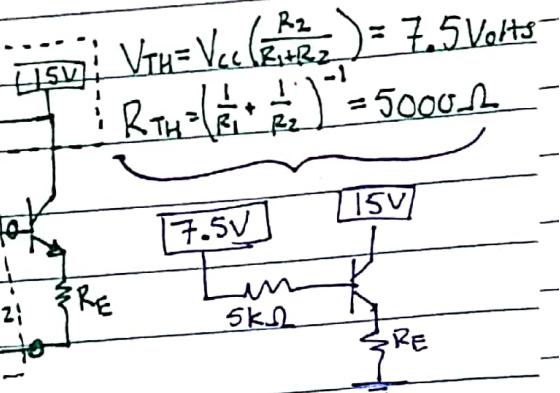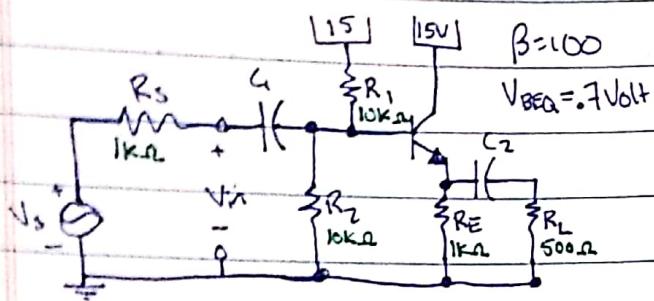

$$7.5 - 5000I_{BQ} - 7 - R_E I_{BQ} = 0$$

$$6.8 - 5000I_{BQ} - 1000(I_B(\beta+1)) = 0$$

$$6.8 - I_{BQ}(5000 - 1000(100+1)) = 0$$

$$I_{BQ} = \frac{6.8}{5000 - 1000(100+1)} = -70.83 \mu A$$

so not in active mode?

56.)

